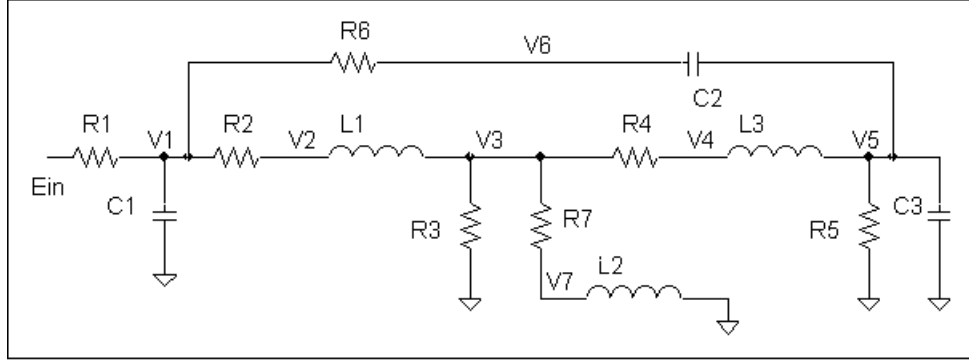


Model of Broadband Pulse Transformer –

In this model, L1 and L3 represent leakage inductance's and L2 is the magnetizing inductance. The capacitors represent interwinding parasitics, and the resistors represent ESR's. The output is taken from C3.



Summing the currents at each node: (Since $V1 = E1 = 1V$, also $I1 = L1$ current = 1A)

$$\text{Node } V1 = E1: \frac{E_{in} - E1}{R1} = i_{C1} + i_{C2} + I1, \quad \text{or} \quad i_{C1} + i_{C2} = \frac{E_{in}}{R1} - \frac{E1}{R1} - I1$$

From this first equation, we fill in the first row of A1 and B2. Since $V1 = E1 = 1V$, and $V5 = E3 = 1V$, the unknowns are:

V2 V3 V4 V6 V7 iC1 iC2 iC3 eL1 eL2 eL3 Column label sequence

$$A1_1 = [0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 0 \quad 0 \quad 0]$$

E1 E2 E3 I1 I2 I3 Ein Column label sequence

$$B2_1 = \begin{bmatrix} \frac{-E1}{R1} & 0 & 0 & -I1 & 0 & 0 & \frac{E_{in}}{R1} \end{bmatrix}$$

Note that we can place E1, E2, I1, I2, etc, in the B2 array since they are known's (all = 1). $E_{in} = 1V$ but can be other constant known values.

This process continues with the 2nd equation from node V2:

$$\text{Node } V2: \frac{E1 - V2}{R2} = I1, \quad \text{or} \quad \frac{V2}{R2} = \frac{E1}{R2} - I1$$

V2 V3 V4 V6 V7 iC1 iC2 iC3 eL1 eL2 eL3 Column label sequence

$$A1_2 = \begin{bmatrix} \frac{1}{R2} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

E1 E2 E3 I1 I2 I3 Ein Column label sequence

$$B2_2 = \begin{bmatrix} \frac{E1}{R2} & 0 & 0 & -I1 & 0 & 0 & 0 \end{bmatrix}$$

The procedure should now be clear. The remaining equations are:

$$\text{Node V3} \quad I_1 = \frac{V_3}{R_3} + I_2 + I_3, \quad \text{or} \quad \frac{V_3}{R_3} = I_1 - I_2 - I_3$$

$$\text{Node V4} \quad \frac{V_3 - V_4}{R_4} = I_3, \quad \text{or} \quad \frac{V_3}{R_4} - \frac{V_4}{R_4} = I_3$$

$$\text{Node V5=E3} \quad I_3 + i_{C2} = \frac{E_3}{R_5} + i_{C3}, \quad \text{or} \quad i_{C2} - i_{C3} = \frac{E_3}{R_5} - I_3, \quad (E_3 = V_5)$$

$$\text{Node V6} \quad \frac{E_1 - V_6}{R_6} = i_{C2}, \quad \text{or} \quad \frac{V_6}{R_6} + i_{C2} = \frac{E_1}{R_6}$$

$$\text{Node V7} \quad \frac{V_3 - V_7}{R_7} = I_2, \quad \text{or} \quad \frac{V_3}{R_7} - \frac{V_7}{R_7} = I_2$$

$U = 5, N = 6$, hence $U+N = 11$ equations are required. We need four more.

$$V_6 = E_2 + E_3; \quad V_2 - V_3 - e_{L1} = 0;$$

$$e_{L2} - V_7 = 0; \quad V_4 - e_{L3} = E_3$$

Simple bookkeeping task: Fill in the columns of A1 from the LH side of these equations.

Note: This circuit is not more complex, the procedure is the same; it's just bigger!

	V2	V3	V4	V6	V7	iC1	iC2	iC3	eL1	eL2	eL3	Column label sequence
	1	2	3	4	5	6	7	8	9	10	11	Column number

$$A1 = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ \frac{1}{R2} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{R3} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{R4} & \frac{-1}{R4} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{R6} & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{R7} & 0 & 0 & \frac{-1}{R7} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \end{bmatrix}$$

Fill the columns of B2 from the RH side of the above equations:.

E1	E2	E3	I1	I2	I3	Ein		B2 column labels
1	2	3	4	5	6	7		Column number

$$B2 = \begin{bmatrix} \frac{-1}{R1} & 0 & 0 & -1 & 0 & 0 & \frac{1}{R1} \\ \frac{1}{R2} & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & \frac{1}{R5} & 0 & 0 & -1 & 0 \\ \frac{1}{R6} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$P = \text{diag}[C1 \ C2 \ C3 \ L1 \ L2 \ L3]$ Same sequence as E1, E2, E3, I1, I2, I3

The ac response plot shows a flat frequency response from about 1KHz to 10MHz (See ac plot following). To prevent a distorted output pulse, the rise time of the input pulse should be greater than

$$tr = \frac{\ln(3)}{\pi \cdot 10\text{MHz}} = 35\text{ns}$$

The rise time of the input pulse is 10ps, hence the output at C3 will be distorted as is shown on the transient response plot.

Output from M-file xfrmrs2.m: Execution time: 14 seconds (2GHz Pentium 4)

