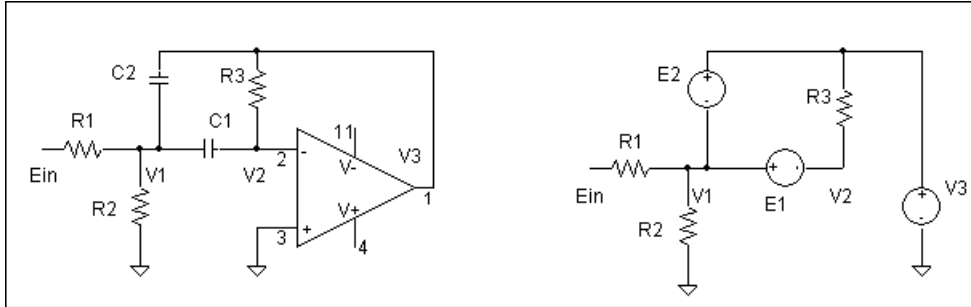


11/15/2006

Improved Multiple Feedback Bandpass Filter Monte Carlo Analysis (MCA) – DS Method

Bandpass Filter

Converted Circuit



Due to the inverting opamp, $V2 = 0$. At first glance there are only two unknown nodes, $V1$ and $V3$. In the converted circuit, $V1 = E1 - V2 = E1 - 0 = 1V$, and $V3$ is the only unknown node. Then $U = 1$, and, since there are two capacitors, $N = 2$, $U + N = 3$ dc equations are required.

At node $V1 = E1$;

$$\frac{E_{in} - E1}{R1} = \frac{E1}{R2} + i_{C1} + i_{C2}, \text{ or } i_{C1} + i_{C2} = -E1 \left(\frac{1}{R1} + \frac{1}{R2} \right) + \frac{E_{in}}{R1}$$

At node $V3 = 0$

$$i_{C1} = \frac{V2 - V3}{R3} = \frac{-V3}{R3}, \text{ or } i_{C1} + \frac{V3}{R3} = 0$$

The last equation is obtained from

$$E2 = V1 - V3 = E1 - V3, \text{ or } V3 = E1 - E2$$

$A1$ and $B2$ are easily constructed from the three equations.

$A1 = \begin{bmatrix} 0 & 1 & 1 \\ \frac{1}{R3} & 1 & 0 \\ 1 & 0 & 0 \end{bmatrix}$	$B2 = \begin{bmatrix} -\left(\frac{1}{R1} + \frac{1}{R2}\right) & 0 & \frac{1}{R1} \\ 0 & 0 & 0 \\ 1 & -1 & 0 \end{bmatrix}$	<div style="display: flex; justify-content: space-around; margin-bottom: 10px;"> $E1$ $E2$ E_{in} </div> <div>Column labels</div>
---	--	---

See M-File mfpbmca.m.

