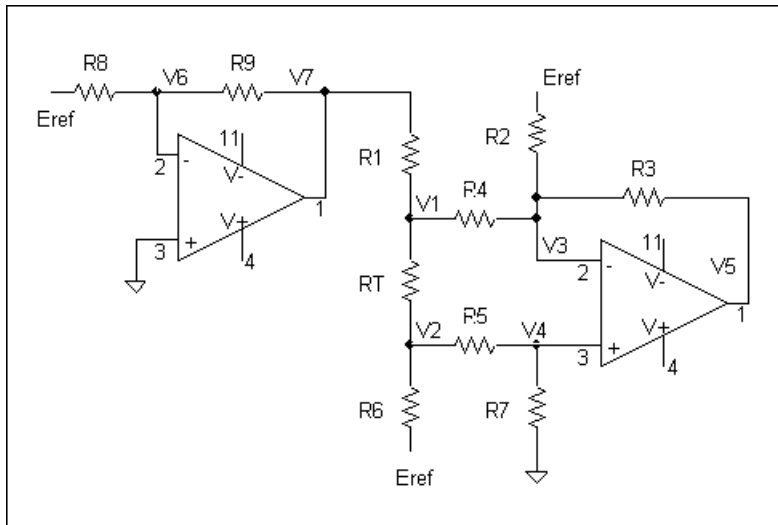


11/15/2006

RTD Circuit (Thermistor is component RT)



Output histograms are shown below for the dc RTD circuit using $N_k = 20,000$ samples. Note that

$$\sqrt{3} \cdot V_{sn} \approx V_{su}; \quad \text{or} \quad \sqrt{3} \cdot (0.217) = 0.376 \approx 0.372$$

Run M_file rtdmca.m

